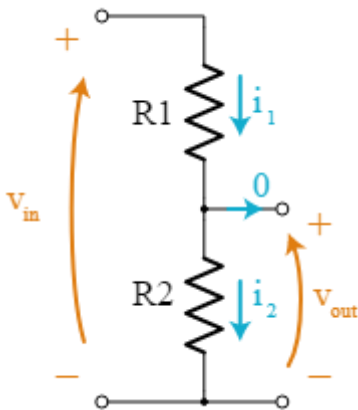
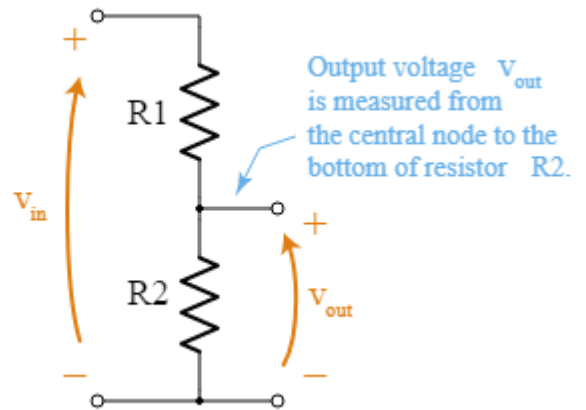


# Voltage Divider

Input voltage  $V_{in}$  is applied to the top and bottom of the series resistors.



$$i_1 = i_2 \quad (\text{series circuit})$$

$$V = iR \quad (\text{Ohms Law})$$

$$V_{in} = i (R_1 + R_2) \rightarrow i = V_{in} / (R_1 + R_2)$$

$$V_{out} = i R_2 \rightarrow V_{out} = (V_{in} / (R_1 + R_2)) R_2 = V_{in} (R_2 / (R_1 + R_2))$$

resistor ratio

$$v_{out} = v_{in} \frac{R_2}{R_1 + R_2}$$

output voltage

input voltage

